



PRINCETON UNIVERSITY  
**SCIENCE OLYMPIAD**  
I N V I T A T I O N A L

2020 Princeton University Invitational Tournament

# Circuit Lab C

## Exam Booklet

- DO NOT BEGIN UNTIL GIVEN PERMISSION
- You will have **50 minutes** to complete the exam || You **may** separate the exam
- For calculation questions, it is **not** required that you show your work, however partial credit will be assigned if correct steps are shown with an incorrect answer.
- Answers must be given with appropriate **significant figures** and **units** to receive full credit.
- All final answers must be placed inside the designated box, including multiple choice.
- **Lab:** You will have up to **20 minutes** to complete **each** lab sections (**2 total**). A proctor will instruct you when it is your turn. You will not be given any replacement components, so be careful not to damage them.
- **Allowed materials:** 3-ring binder, writing utensils, two calculators, basic multimeter
- **Tie-breaker order:** 9, 11, 13, 26, 28, 32, 39, 41

**Competitors:** \_\_\_\_\_  
\_\_\_\_\_

**School Name:** \_\_\_\_\_

**Team Number:** \_\_\_\_\_

**Rank:** \_\_\_\_\_

**Score:** \_\_\_\_\_

Kevin Hao<sup>1</sup>, Asher Noel<sup>2</sup>, Megan Pramojaney<sup>3</sup>

<sup>1</sup>University of Florida - BS Biology '21, MD '24

<sup>2</sup>Harvard College – BA Computer Science and Statistics '23

<sup>3</sup>University of North Carolina Chapel Hill – BS Physics '23

[kevin@floridascienceolympiad.org](mailto:kevin@floridascienceolympiad.org)

[ashernoel@college.harvard.edu](mailto:ashernoel@college.harvard.edu)

[pramoj23@live.unc.edu](mailto:pramoj23@live.unc.edu)

This page is for administrative use only. DO NOT WRITE ON THIS PAGE.

<b>Page Number</b>	<b>Possible Score</b>	<b>Your Score</b>
3	20	
4	24	
5	26	
6	38	
7	20	
8	28	
9	24	
10	28	
LAB 1	36	
LAB 2	40	
<b>Total</b>	<b>284</b>	

1. Part 1: Order the seven scientists in the rules by the ascending date of their crowning contribution to this field. Part 2: Write the year of each scientist's crowning contribution next to their name. 1 pt for correct, -1 pt for incorrect, 0 pts for blank. <sup>2</sup> (10 pts; 3, 7)

*Example Box Format*

<i>Last Name (Year)</i>	1750 →	→	→	→
2020 ←	←	←	←	←

2. Short Response: Who won the War of the Currents: Edison or Tesla? Make a strong claim, support your idea with verifiable evidence and analysis, and write clearly. <sup>2</sup> (4 pts; 1, 1, 1, 1)

---

---

---

---

---

---

---

---

---

---

3. Long Response: Of the scientists listed in the rules, who most deserved to win a Nobel Prize, assuming the Nobel Prize were established in 1700? Make a strong claim, support your idea with verifiable evidence and analysis, and write clearly. <sup>2</sup> (6 pts; 1, 2, 2, 1)

---

---

---

---

---

---

---

---

---

---

---

---

---

---

---

---

---

---

---

---

---

---

---

---

4. [A] Which could be performed to simplify the circuit? <sup>1</sup> (2 pts)

- A. Y-to- $\Delta$                       B.  $\Delta$ -to-Y  
 C. Either                              D. Neither

5. [A] Determine  $V_o$ . <sup>1</sup> (2 pts)

- A. 15 V                                  B. 18 V  
 C. 22 V                                  D. 35 V

6. [B] Determine  $V_x$ . <sup>1</sup> (2 pts)

- A. 4 V                                    B. 6 V  
 C. 7 V                                    D. 8 V

7. [B] Determine  $V_y$ . <sup>1</sup> (2 pts)

- A. 4 V                                    B. 6 V  
 C. 7 V                                    D. 8 V

8. [B] Determine  $i$ . <sup>1</sup> (2 pts)

- A. 0.5 A                                  B. 1.0 A  
 C. 1.5 A                                  D. 3.0 A

9. [C] Determine the resistance of the device. <sup>1</sup> (2 pts) (TB#1)

- A. 27  $\Omega$                                   B. 27 k $\Omega$   
 C. 54  $\Omega$                                   D. 54 k $\Omega$

10. [D] Determine the resistance of the device. <sup>1</sup> (2 pts)

- A. 3.6 k $\Omega$                                   B. 4.1 k $\Omega$   
 C. 4.9 k $\Omega$                                   D. 5.6 k $\Omega$

11. [E] Determine the polarities. (Choose all that apply) <sup>1</sup> (2 pts) (TB#2)

- A. W = North                              B. X = North  
 C. Y = North                              D. Z = South

12. [F] Determine the required input (A,B,C) to achieve X=1. <sup>1</sup> (2 pts)

- A. 1, 0, 1                                  B. 0, 0, 1  
 C. 1, 1, 1                                  D. 0, 1, 1

13. [G] Determine the corresponding logic gate. <sup>1</sup> (2 pts) (TB#3)

- A. AND                                      B. OR  
 C. XOR                                      D. NOR

14. All combinational logic functions can be realized by: <sup>1</sup> (2 pts)

- A. OR only                                  B. XOR only  
 C. AND only                                  D. NOR only


15. A bulb in a staircases has two switches, one switch being at the ground floor and the other one at the first floor. The bulb can be turned ON and also can be turned OFF by one of the switches irrespective of the state of the other switch. The logic of switching of the bulb represents: <sup>1</sup> (2 pts)

- A. an AND gate                              B. an XOR gate  
 C. an OR gate                                D. an NAND gate

A																			
B																			
C	<table border="1" data-bbox="1349 625 1516 842"> <thead> <tr> <th><math>i</math> (mA)</th> <th><math>v</math> (V)</th> </tr> </thead> <tbody> <tr><td>-4</td><td>-108</td></tr> <tr><td>-2</td><td>-54</td></tr> <tr><td>2</td><td>54</td></tr> <tr><td>4</td><td>108</td></tr> <tr><td>6</td><td>162</td></tr> </tbody> </table>	$i$ (mA)	$v$ (V)	-4	-108	-2	-54	2	54	4	108	6	162						
$i$ (mA)	$v$ (V)																		
-4	-108																		
-2	-54																		
2	54																		
4	108																		
6	162																		
D	<table border="1" data-bbox="1386 877 1533 1094"> <thead> <tr> <th><math>v</math> (V)</th> <th><math>p</math> (mW)</th> </tr> </thead> <tbody> <tr><td>-10</td><td>17.86</td></tr> <tr><td>-5</td><td>4.46</td></tr> <tr><td>5</td><td>4.46</td></tr> <tr><td>10</td><td>17.86</td></tr> <tr><td>15</td><td>40.18</td></tr> <tr><td>20</td><td>71.43</td></tr> </tbody> </table>	$v$ (V)	$p$ (mW)	-10	17.86	-5	4.46	5	4.46	10	17.86	15	40.18	20	71.43				
$v$ (V)	$p$ (mW)																		
-10	17.86																		
-5	4.46																		
5	4.46																		
10	17.86																		
15	40.18																		
20	71.43																		
E																			
F																			
G	<table border="1" data-bbox="1187 1682 1463 1936"> <thead> <tr> <th colspan="2">Input</th> <th>Output</th> </tr> <tr> <th>A</th> <th>B</th> <th>Q</th> </tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>0</td></tr> </tbody> </table>	Input		Output	A	B	Q	0	0	0	0	1	1	1	0	1	1	1	0
Input		Output																	
A	B	Q																	
0	0	0																	
0	1	1																	
1	0	1																	
1	1	0																	



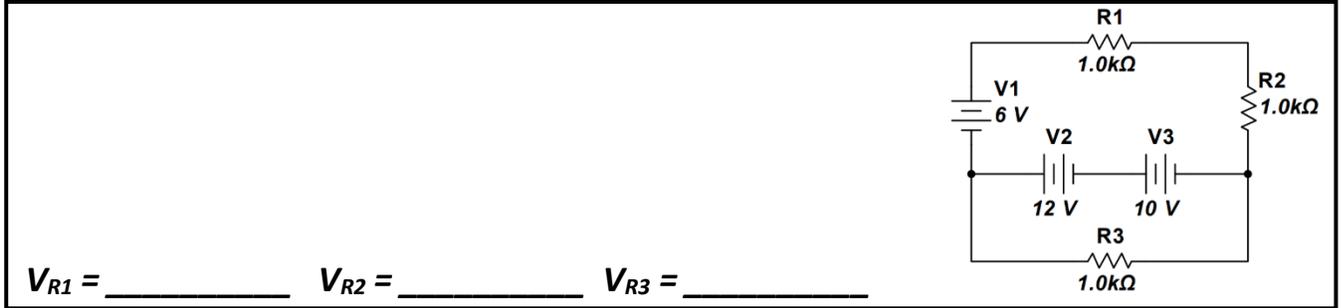
27. Determine the voltage drop across each resistor. Provide your answers to 3 significant figures. <sup>1</sup> (6 pts; 2, 2, 2)




28. Determine the current  $I_o$  and the voltage  $V_o$ . Provide your answers to 3 significant figures. <sup>1</sup> (12 pts; 6, 6) (TB#5)



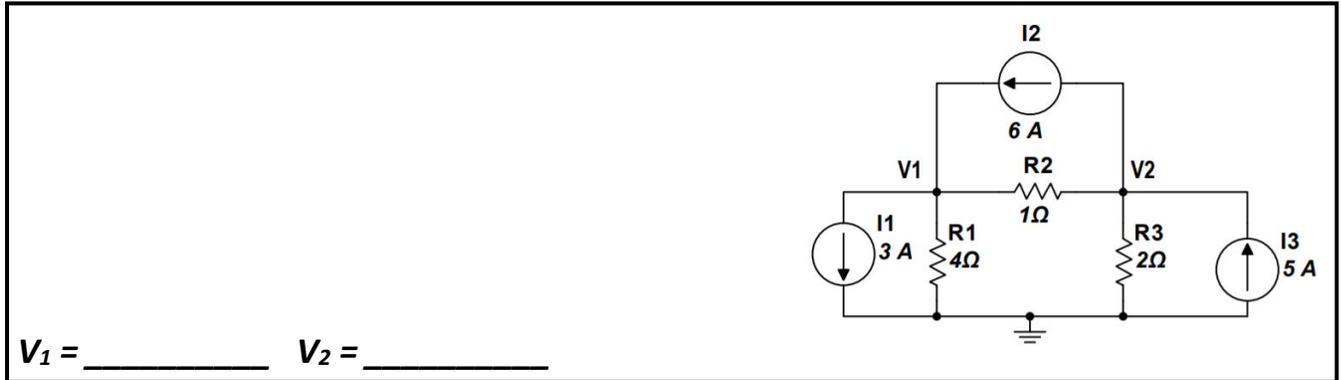29. Determine the node voltages  $V_1$  and  $V_2$ . Provide your answers to 3 significant figures. <sup>1</sup> (8 pts; 4, 4)



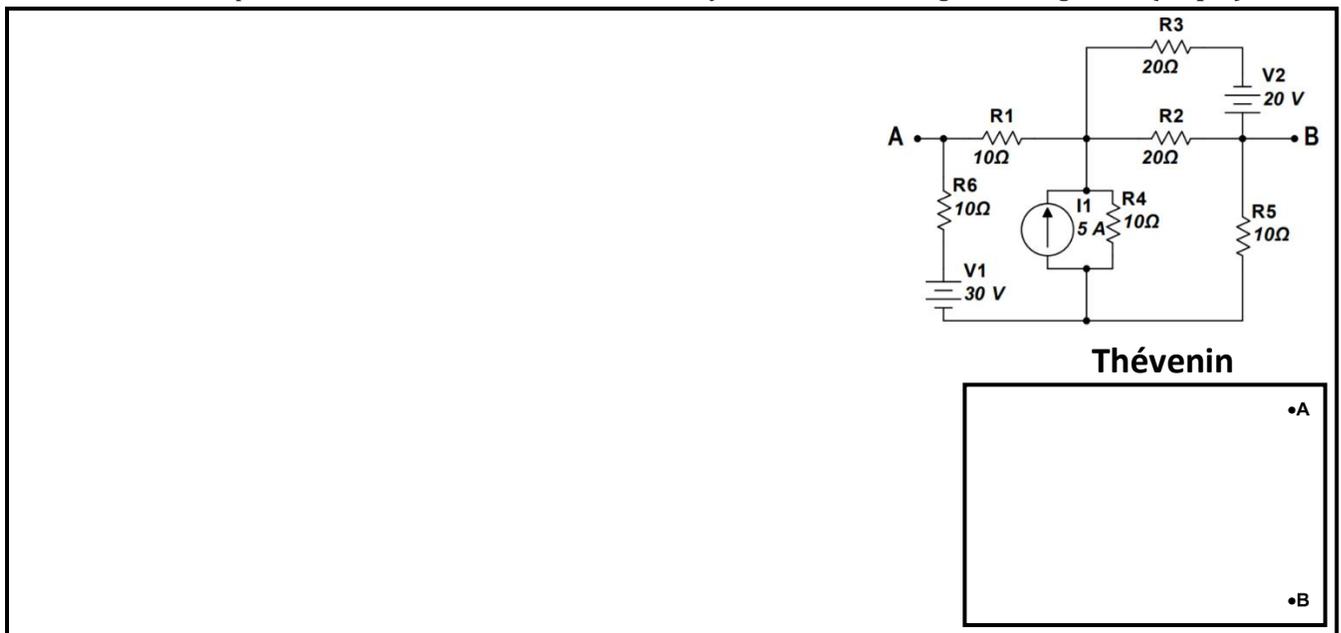30. Find the Thevenin equivalent between nodes A and B. Provide your answers to 3 significant figures. <sup>1</sup> (12 pts)



31. Pictured is an instrument designed to measure current. Answer the following questions: <sup>3</sup> (10 pts; 4, 1, 1, 4)

- Name components A-D in the diagram. (4 pts)
- State the name of the instrument. (1 pt)
- Indicate whether you would connect it to a circuit in series or parallel. (1 pt)
- Consider one of the earliest versions of this type of instrument, where the needle pictured would deflect on the linear scale by an angle  $\theta$  given by  $\theta = \tan^{-1} \frac{B}{B_H}$ , where B is the magnetic field at the center of the coil in the device and  $B_H$  is the horizontal component of the Earth's magnetic field at a given point on earth. Suppose that the needle is deflected  $30^\circ$ . Given that the coil in the device has 350 turns and a radius of 2.5 cm, calculate the current flowing through the coil in terms of  $B_H$ . Assume  $B_H$  is given in its SI base unit(s). (4 pts)

**A:** \_\_\_\_\_

**B:** \_\_\_\_\_


**C:** \_\_\_\_\_

**D:** \_\_\_\_\_

**Name:** \_\_\_\_\_

**(Circle one):** ( Series | Parallel )

**I =** \_\_\_\_\_

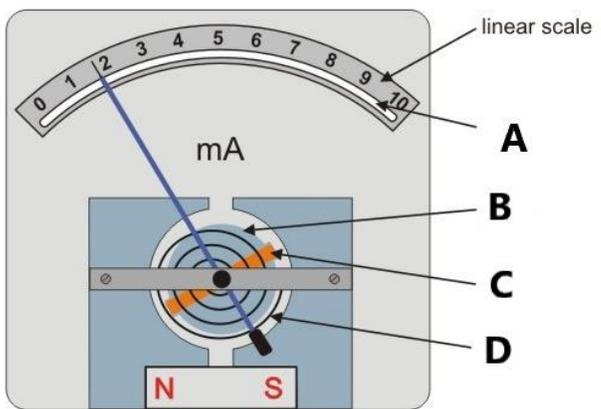


32. Perform the following for the transistor circuit shown below given that the voltage at the base of the transistor is 5.33 V and  $\beta = 100$ . Assume that the transistor has a forward voltage drop of 0.7 V. Provide your answers to 3 significant figures. <sup>3</sup> (10 pts; 2, 2, 6) (TB#6)

- State the junction type of the transistor? (2 pts)
- State the mode the transistor is in. (2 pts)
- Find the Q-point of the transistor by calculating  $I_{EQ}$  and  $V_{CEQ}$ . (6 pts; 3, 3)

**Junction type =** \_\_\_\_\_

**Transistor Mode =** \_\_\_\_\_

**Q-point:** \_\_\_\_\_

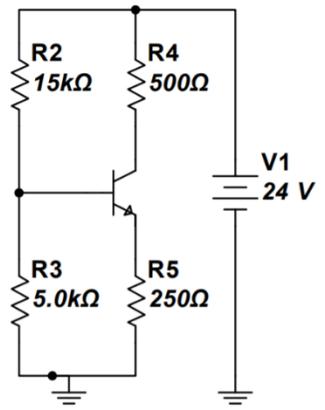



36. A charged particle moving through a magnetic field at right angles to the field with a speed of 22.7 m/s experiences a magnetic force of  $2.58 \times 10^{-4} \text{ N}$ . Determine the magnetic force on an identical particle when it travels through the same magnetic field with a speed of 5.54 m/s at an angle of  $27.2^\circ$ .<sup>1</sup> (8 pts)

$F =$  \_\_\_\_\_

37. State DeMorgan's Theorem. Then apply it to draw the appropriate gates and their Boolean expressions in the spaces provided.<sup>1</sup> (8 pts; 2, 4, 2)

\_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_

$\overline{AB}$ 	=	<p>_____</p> <p>A _____</p> <p>B _____</p> <p style="text-align: right;">→</p>
$\overline{A + B}$ 	=	<p>_____</p> <p>A _____</p> <p>B _____</p> <p style="text-align: right;">→</p>

38. Draw two possible logic gate diagrams mapping the expression  $Z = \bar{A} \cdot \bar{B} \cdot (C + D)$ .<sup>1</sup> (8 pts; 4, 4)

39. Name the circuit and complete the truth table. <sup>1</sup> (10 pts; 2, 8) (TB#7)

Clock	D	Q	Q'
↓ >> 0	0		
↑ >> 1	0		
↓ >> 0	1		
↑ >> 1	1		

**Logic Gate Configuration:** \_\_\_\_\_

40. Draw an electrical control diagram using three 3-way (SPDT) and one 4-way (DPDT) switches that controls two lights in accordance to the truth table provided. Use a 5V DC light and a 5V DC source. Label the switches (S1, S2, and S3) and light (L1). Examples of SPDT and DPDT switches in the OFF (0) position are provided. <sup>1</sup> (10 pts)

S1	S2	S3	L1
0	0	0	1
1	0	0	0
0	1	0	0
0	0	1	0
1	1	0	1
1	0	1	1
0	1	1	1
1	1	1	0

41. Draw magnetic field lines (including arrows) for the pair of magnets shown below. Indicate the direction of motion for each magnet if they were not held in place by drawing an arrow in each box above the magnets. <sup>1</sup> (8 pts; 6, 2) (TB#8)

**LAB 1 (Circuit Diagnostics):** At this station, you will analyze three circuits, determine the problem with each, and propose a solution to fix them. <sup>1</sup> **(36 pts total)**

42. **Circuit 1** is meant to produce light, but the LED currently connected to the circuit is not turning on. Using your voltmeter to take measurements of voltage only from the labeled leads, determine why the LED is not turning on. Then perform the following: <sup>1</sup> **(20 pts)**

- **Draw up to two unique** solutions to fix the circuit using the additional components provided. Each solution should only have ONE modification. HINT: any color LED is acceptable as long as light is produced. **(12 pts; 6, 6)**
- **Explain how** each solution fixes the initial problem. **(8 pts; 4, 4)**

---

---

---

---

---

---

43. **Circuit 2** is meant to power all the LEDs with equal brightness, but the LEDs are varying in brightness. Determine the problem with the circuit and then perform the following: <sup>1</sup> **(8 pts)**

- Redraw Circuit 2 **using the same components**. **(6 pts)**
- **Explain how** your new schematic fixes the initial problem. **(2 pts)**

---

---

---

---

---

---

---

44. **Circuit 3** is a DC gain op-amp circuit that is supposed to produce a 10V output voltage, but only 5V is being measured. Determine the problem with the circuit and then perform the following: <sup>1</sup> **(8 pts)**

- **Explain** the problem with the circuit. **(6 pts)**
- Determine if it is possible to fix the circuit to achieve the desired output using the provided components. **(2 pts)**

---

---

---

**Possible to fix? (Circle one): ( Yes | No )**

**LAB 2 (Digital Logic):** At this station, you will first **analyze** a circuit. On the breadboard provided, there is a pre-built logic gate circuit. <sup>1</sup> **(40 pts total)**

45. **[Analysis]** Perform the following for the circuit constructed on the breadboard: <sup>1</sup> **(40 pts)**

- Complete a truth table for the circuit using the template provided. **(4 pts)**
- Draw a logic gate diagram. Each gate constructed in the circuit should be included. Label each gate. **(12 pts)**
- Draw a circuit diagram. Include component values where appropriate. You may represent the inputs constructed using press buttons on the breadboard as SPST or SPDT switches. Label A, B, C, and Q. **(24 pts)**

<b>Logic Diagram</b>	A	B	C	Q
	0	0	0	
	1	0	0	
	0	1	0	
	0	0	1	
	1	1	0	
	0	1	1	
	1	0	1	
	1	1	1	

**Circuit Diagram**